

## Lecture 4: More Lab 1

David Black-Schaffer  
davidbbs@stanford.edu  
EE183 Spring 2003

## Overview

- Hardware vs. Software
  - Think about how many adders you are creating
  - Hierarchical design is good for both **scalability** and **debugging!**
- Output to VGA
  - Double-buffering via dual BRAMs
  - Take the MSBs of the VGA position to index into BRAMs (*understand this!*)
- FSMs
  - Inferred latches: bad; Knowing your hardware: good

EE183 Lecture 4 - Slide 2

## Logistics

- Any questions?
  - Lab 1 requirements clear?
  - We'll be talking about RAM, FSMs, and VGA today
- Finished the tutorial yet?
  - Due **TONIGHT** by midnight
    - email URL for your PDF to Joel
    - See "Tao of EE183" on web
    - Tutorial is a mini-writeup (not a lot of text)
- Start on pre-lab for lab 1
  - Complete Design section
  - FSMs and block diagram
  - The more you do here the easier lab 1 will be...

EE183 Lecture 4 - Slide 3

## Lab 1 Requirements

- Implement a VGA Game of Life
  - 64x64 wrap-around grid
  - Update speed 2-4Hz
  - Gamepad editor for initial state and edit/run mode select with a blinking cursor
- Optional (encouraged and easy)
  - Speed-up button
  - Background image

EE183 Lecture 4 - Slide 4

## Hierarchical Design

- Two main modes:
  - Edit
  - Run
- Two main modules?
- Master Control module?
- Think about hierarchical FSMs for both design & debugging
  - What should the top level FSM do?
  - What should the lower-level FSMs be?
  - Can the enables/resets help?
  - Do you need other signals? (done? slow clock?)

EE183 Lecture 4 - Slide 5

## BRAM stores game state

- Each BRAM is 4Kbits
  - So we can have a 64x64x1 game board
  - Use CoreGen and create it as 4Kx1 and use the **concatenation of the row and column as the index**: {X,Y} where X, Y are 6-bit (0..64)
  - Is this clear?
- But, we need two of them
  - One to store current state
  - and one to write the next state into.

EE183 Lecture 4 - Slide 6

## Reading from a RAM

- How do you read from a RAM?

```
case(state)
`READ_UP:
    bram_address = {X,Y-1};
    bram_enable = 1;
    next_state = GET_UP;
    neighbor_counter_enable = 0;
`GET_UP:
    bram_address = 12'b0; //WHY!?
    bram_enable = 0;
    next_state = READ_LEFT;
    neighbor_counter_enable = bram_out;
`READ_LEFT:
    ...
```

Address in here

Data out  
One (?) cycle later!

EE183 Lecture 4 - Slide 7

## Next State FSM

- Think about the algorithm for one cell
  - How would you do this in C?
    - Iterate over every cell and look at the neighbors.
  - Remember this is in hardware!
  - Speed vs. area is always the tradeoff

How many adders? Does it matter?

EE183 Lecture 4 - Slide 8

### C Algorithm

```

for x = 0..63 {
  for y = 0..63 {
    neighbors = 0;
    // Look at all the neighbors
    if (current_state[x-1][y])
      neighbors++;
    if (current_state[x-1][y-1])
      neighbors++;
    if (current_state[x][y-1])
      neighbors++;
    ...
    if (current_state[x][y] == 0)
      if (neighbors == 2) || (neighbors == 3)
        next_state[x][y] = 1;
      else if (neighbors == 3)
        next_state[x][y] = 1;
      else
        next_state[x][y] = 0;
  }
}

```

What is a for loop in hardware?  
A counter with a comparator for the end value?  
But it will be enabled by a FSM!

How many adders do you have here?  
Two for each neighbor? Or re-use two?

How do you store the number of neighbors?  
A counter? Controlled by the FSM?

How do you swap the next\_state and current\_state after each iteration? MUX?

EE183 Lecture 4 - Slide 9

### Verilog State Machine(s)

```

always @(current_state_q or ??)
begin
  case(current_state_q)
    CHECK_LEFT: begin
      next_state_d = ??
    end
    CHECK_UPLEFT: begin
      next_state_d = ??
    end
    CHECK_UP: begin
      next_state_d = ??
    end
    CHECK_UP_RIGHT: begin
      next_state_d = ??
    end
    .
    .
    .
    UPDATE_CELL: begin
      next_state_d = ??
    end
  endcase
end

```

How do you get the current\_state[x-1][y]?

How do you keep track of the neighbor count?

How does your memory access fit in here?

How do you change the x and y for each cell?

EE183 Lecture 4 - Slide 10

## Double Buffering

- We need to have the VGA logic switch between the two BRAMs depending on which one is the current complete game state.
  - Standard technique in many areas but specifically graphics.
  - current\_bram vs. next\_bram
- Make this a self-contained module so you only have one current output and the VGA doesn't have to know which BRAM to use. Standard OOP practice. (what will deal with the switching?)

EE183 Lecture 4 - Slide 11

## How do we display?

- When it is refreshing, the VGA needs a data element every clock (remember it gives you the X and Y and you give it the color - it always needs some color)
  - Whenever the VGA is valid we **MUST** provide it with a color
  - We could coordinate the game state updates to occur around the VGA screen refreshes but this is a pain.
- Instead use a **dual port memory** and use one port for the game state updates and one for display.
  - Dual port memories are already implemented in BRAMs so we might as well use it.
  - Port A is for updating the game state (FSM control)
  - Port B is for the VGA color output (VGA control)


EE183 Lecture 4 - Slide 12

## Key VGA Points

- Two concepts here:
  - Double Buffering: draw the next state into one memory while displaying from the first, then switch
  - Dual-port RAM: use one port for the VGA to draw from and the other for the next\_state FSM to update the game state
- These work together to make this fast and easy

EE183 Lecture 4 - Slide 13

## Double Buffering & Dual Ports

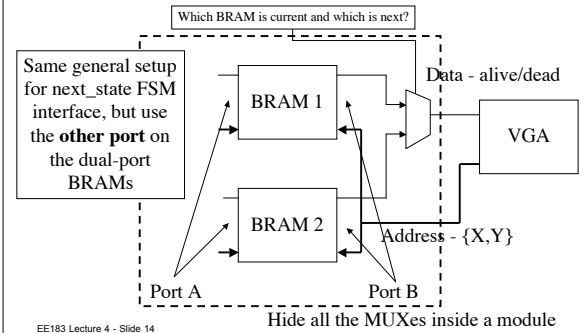


## How do we actually generate the image?

- Split the screen up into a 64x64 grid
  - Fine if it is in top left corner
  - Can you use a divider?
    - How do you divide by a power of 2?
- Could directly draw to the screen
- Could use TCGROM
  - Maybe change one of the characters to a solid block and then an outline block so there is a grid? Cheap ways to make a grid?

EE183 Lecture 4 - Slide 15

## VGA

 

- We want 64x64
- No dividers
- Okay if it doesn't fill the screen

Bit 0: divide in half  
 Bit 1: divide in quarters  
 Bit 2: divide in eights

...

EE183 Lecture 4 - Slide 16

## Optional Fun Things

- Display the number of iterations
- Clear-screen button
- Random start state button
  - LFSR seeded by free-running counter
- Fast-forward
- Interesting initial state
  - Use Memutils.zip to load a state into the BRAM via a .coe file
- Background image
  - Simply use a third BRAM and display it when the cell is off

EE183 Lecture 4 - Slide 17

## FSM Review

A Finite State Machine is simply a **state register** that holds the current state and some **combinational logic** which calculates the next state and outputs based on the current state and the inputs.

- A feedback system which updates on each clock

EE183 Lecture 4 - Slide 18

## What is it really?

- A bunch of MUXes which select the next state & outputs based on the current state (FFs) & inputs.
- Keep this in mind when writing your verilog.

EE183 Lecture 4 - Slide 19

## Inferred Latch Review

An inferred latch occurs when **you fail to define all the outputs** for a given path through your logic and the tools instead try to remember the previous output to make up for this.

- All outputs have to be defined at all times in real hardware

EE183 Lecture 4 - Slide 20

## What is it really?

- A mux where you haven't defined one of the inputs so it remembers the last value and loops it around.
- Make sure you know and state what all outputs should be at all times.

EE183 Lecture 4 - Slide 21

```
always @(current_state_q or button)
begin
  case(current_state_q)
  `STOP: begin
    go = 1'b0;
    if (button) begin
      next_state_d = `GO;
    end
    else begin
      next_state_d = `STOP;
    end
  end
  `GO: begin
    go = 1'b1;
    if (button) begin
      next_state_d = `STOP;
    end
    else begin
      next_state_d = `GO;
    end
  end
  default: begin
    go = 1'b0;
    next_state_d = `STOP;
  end
end
```

The next state must **ALWAYS** be defined.

Any output must be defined in **EVERY** state.

If any states are ever not used they **MUST** be included in a **default** statement.

**an else for every if  
a default for every case  
every output must be defined in every state**

## Inferred Latches

- So why are they bad, really?
  - Hard to debug (hidden states in your logic)
    - You intend a MUX and get a MUX with memory
    - You intend a certain number of states but end up with states with memories (i.e., sub-states)
    - You weren't really thinking things all the way through or you wouldn't have had them!
  - Hard to optimize speed (hidden states in your logic)
    - What is your critical path? Depends on how many levels of logic between FFs.

EE183 Lecture 4 - Slide 23

## Timing

- What limits our speed?
- RTL design - Register Transfer Logic
  - Speed limited by the time it takes to get from one register (flip flop) to another
  - State machines and pipeline data stages
- What gets in the way?
  - Combinational logic delay
  - Routing delay
  - FF setup and hold time requirements
  - Clock skew and delay

EE183 Lecture 4 - Slide 24

## Combination Logic Delay

- Time to get through gates
  - The more gates (more complicated logic) the slower
  - One-hot encoding
- Well, sort of:
  - FPGA doesn't have "gates" we have those 4-input LUTs (look-up-tables)
  - All functions of 4 inputs or less are the same speed
  - >4 inputs and we have to hook up multiple CLBs (routing delay)

EE183 Lecture 4 - Slide 25

## Routing Delay

- This can be (IS!) the real killer
- FPGA wiring slow compared to ASIC
  - Lots of switches to go through
  - Wires don't go exactly where you want
- Routing can be ~50% of your total delay
- Manual placement? NP-hard problem?
- Hope the tools work well!

EE183 Lecture 4 - Slide 26

## Lecture 4 Key Points

- VGA gives you an X and Y coordinate and you set the color.
- Double buffering: calculate from one memory into the other
- Calculate-next-state FSM looks at all the neighbors to figure out alive/dead
- Logistics
  - **Prelab must contain all your FSM description (pseudo-verilog) and block diagrams** (don't waste your time drawing pictures in Word)

EE183 Lecture 4 - Slide 27