



LOGIC FOUNDRY Why Custom Hardware?

- Size – Area constraints may force us to use a specific item rather than a general solution
 - Smart Card
- Cost – mass production of specific item may be cheaper than utilizing a general solution
 - Coke Machine???
 - Most of these apps are generally done by low-cost microprocessors.
- Power – A general solution might require more power than we have available on our system
 - Cell Phone
- Or ...

Rincon Research Corporation - FPGA Development 2

LOGIC FOUNDRY Performance

Rincon Research Corporation - FPGA Development 3

LOGIC FOUNDRY Some Challenges

- How do we take something running in software and make it fast?
 - Algorithmic changes
 - By FAR, the most significant
 - Architecture choices
 - Implementation choices
 - Synthesis Optimizations
 - Place and Route Optimizations

Rincon Research Corporation - FPGA Development 4

Algorithmic Changes

- Algorithms are generally developed to function on a general-purpose computer
 - Sequential algorithms
 - Floating point precision
 - Memory access is either un-optimized or optimized for cache accesses – but still sequentially
 - A sequential algorithm sees no difference between interacting with 1 or 1000 arrays of data
- In order to work effectively in hardware:
 - Parallel algorithms
 - Stream of concurrent processes
 - Many identical components doing different solutions
 - Integer precision
 - Optimized for finite memory sizes and ports
 - Removal of processing "walls" where all processing is forced to wait for the completion of an event before proceeding

Rincon Research Corporation - FPGA Development 5

LFSR Example

Fibonacci vs. Galois Linear Feedback Shift Register (LFSR)

Rincon Research Corporation - FPGA Development 6

Turbo Decoder Example

Rincon Research Corporation - FPGA Development 7

Architecture Choices

- A Brief survey of Verilog blocking vs. nonblocking assignments
- Pipelining
 - Register Retiming
- State Machine Implementations
 - Structure
 - Encoding
- FPGA Details

Rincon Research Corporation - FPGA Development 8

LOGIC FOUNDRY Blocking vs. Nonblocking Assignments

- Verilog has 2 types of assignments to a register datatype
 - Blocking (a = b)
 - Nonblocking (a <= b)
- Blocking Assignments
 - Performed immediately (simulation blocks)
- Nonblocking Assignments
 - Performed after all active events in the event queue

Rincon Research Corporation - FPGA Development 9

LOGIC FOUNDRY Simplified Verilog Simulation Reference Model

In all the examples that follow, T refers to the current simulation time, and all events are held in the event queue, ordered by simulation time.

```

while (there are events) {
  if (there are active events) {
    E = any active event;
    if (E is an update event) {
      update the modified object;
      add evaluation events for sensitive processes to event queue;
    }
    else ( // this is an evaluation event, so ...
      evaluate the process;
      add update events to the event queue;
    )
  }
  else if (there are nonblocking update events) {
    activate all nonblocking update events;
  }
  else {
    advance T to the next event time;
    activate all inactive events for time T;
  }
}

```

Rincon Research Corporation - FPGA Development 10

LOGIC FOUNDRY References

- Cliff Cummings - <http://www.sunburst-design.com/papers/>
 - Nonblocking Assignments in Verilog Synthesis, Coding Styles That Kill!
 - Verilog Nonblocking Assignments With Delays, Myths & Mysteries

Rincon Research Corporation - FPGA Development 11

LOGIC FOUNDRY Difference between blocking and nonblocking


```

always @ (posedge clk)      always @ (posedge clk)
begin                       begin
  b = a;                   b <= a;
  c = b;                   c <= b;
end                         end

```

Rincon Research Corporation - FPGA Development 12

 - Pipelining
 - explicitly by the designer
 - automatically by the synthesis tool
- Consider a population counter



```

module test (a, pop, clk, rst);
input [32:0] a;
input clk, rst;
output [6:0] pop;
reg [6:0] pop;

always @ (posedge clk or posedge rst) begin
if (rst) begin
pop <= 0;
end
else begin
pop <= a[0] + a[1] + a[2] + a[3] + a[4] + a[5] + a[6] + a[7] +
a[8] + a[9] + a[10] + a[11] + a[12] + a[13] + a[14] + a[15] +
a[16] + a[17] + a[18] + a[19] + a[20] + a[21] + a[22] + a[23] +
a[24] + a[25] + a[26] + a[27] + a[28] + a[29] + a[31] + a[31];
end
end
endmodule
    
```

```

module test (a, pop, clk, rst);
input [32:0] a;
input clk, rst;
output [6:0] pop;

reg [2:0] p1,p2,p3,p4,p5,p6,p7,p8,p9,p10,p11;
reg [4:0] q1,q2,q3,q4;
reg [5:0] r1,r2;
reg [6:0] pop;

always @ (posedge clk or posedge
rst) begin
if (rst) begin
pop <= 0;
end
else begin
p1 <= a[0] + a[1] + a[2];
p2 <= a[3] + a[4] + a[5];
p3 <= a[6] + a[7] + a[8];
p4 <= a[9] + a[10] + a[11];
p5 <= a[12] + a[13] + a[14];
p6 <= a[15] + a[16] + a[17];
p7 <= a[18] + a[19] + a[20];
p8 <= a[21] + a[22] + a[23];
p9 <= a[24] + a[25] + a[26];
p10 <= a[27] + a[28] + a[29];
p11 <= a[31] + a[31];
q1 <= p1 + p2 + p3;
q2 <= p4 + p5 + p6;
q3 <= p7 + p8 + p9;
q4 <= p10 + p11;
r1 <= q1 + q2;
r2 <= q3 + q4;
pop <= r1 + r2;
end
end
endmodule
    
```

```

module test (a, pop, clk, rst);
input [32:0] a;
input clk, rst;
output [6:0] pop;

reg [2:0] p1,p2,p3,p4,p5,p6,p7,p8;
reg [4:0] q1,q2;
reg [6:0] pop;

always @ (posedge clk or posedge rst)
begin
if (rst) begin
pop <= 0;
end
else begin
p1 <= a[0] + a[1] + a[2] + a[3];
p2 <= a[4] + a[5] + a[6] + a[7];
p3 <= a[8] + a[9] + a[10] +
a[11];
p4 <= a[12] + a[13] + a[14] + a[15];
p5 <= a[16] + a[17] + a[18] + a[19];
p6 <= a[20] + a[21] + a[22] + a[23];
p7 <= a[24] + a[25] + a[26] + a[27];
p8 <= a[28] + a[29] + a[30] + a[31];
q1 <= p1 + p2 + p3 + p4;
q2 <= p5 + p6 + p7 + p8;
pop <= q1 + q2;
end
end
endmodule
    
```

LOGIC FOUNDRY **Population Count Retimed**

```

module test (a, pop, clk, rst);
input [32:0] a;
input clk, rst;
output [6:0] pop;
reg [6:0] pop;
reg [6:0] p1, p2, p3, p4;

always @ (posedge clk or posedge rst) begin
if (rst) begin
pop <= 0;
p1 <= 0;
p2 <= 0;
p3 <= 0;
end
else begin
p1 <= a[0] + a[1] + a[2] + a[3] + a[4] + a[5] + a[6] + a[7] +
a[8] + a[9] + a[10] + a[11] + a[12] + a[13] + a[14] + a[15] +
a[16] + a[17] + a[18] + a[19] + a[20] + a[21] + a[22] + a[23] +
a[24] + a[25] + a[26] + a[27] + a[28] + a[29] + a[31] + a[31];
p2 <= p1;
p3 <= p2;
p4 <= p3;
pop <= p4; // pop <= p3; pop <= p2; pop <= p1;
end
end
endmodule

```

Rincon Research Corporation - FPGA Development 17

LOGIC FOUNDRY **Population Count Example Times**

- Solo pop count => 148 MHz
- Pipelined version 1 => 296 MHz
- Pipelined version 2 => 279 MHz
- Retimed pop <= p4; => 308 MHz
- Retimed pop <= p3; => 316 MHz
- Retimed pop <= p2; => 328 MHz
- Retimed pop <= p1; => 293 MHz

Rincon Research Corporation - FPGA Development 18

LOGIC FOUNDRY **State Machines**

- Use one sequential always block for next state assignment:
 - Typically 3 lines of code

```

always @ (posedge clk or negedge rst_n)
if (!rst_n) state <= IDLE;
else state <= next;

```
- Put the state machine outputs in a separate combinational always block
- This 2-block style is efficient because output assignments are only required to be listed once for each state in the case statement
- Avoid Verilog race conditions
 - Code all sequential always blocks using non-blocking assignments
 - Code all combinational blocks using blocking assignments

Rincon Research Corporation - FPGA Development 19

LOGIC FOUNDRY **State Machine Encoding**

- In Verilog, use parameters as state assignments rather than 'defines
 - 'defines are global
 - This avoids redefinition warnings when multiple state machines exist in a compilation
- Use one-hot encoding for high-performance state machines
 - This technique uses more registers, but simplifies next-state logic
 - That said, the number of excess registers is typically trivial when compared to the controlled datapath
 - In Verilog, using reverse **case** statement ensures inference of efficient comparison logic that only does 1-bit comparisons against the onehot bits of the **state** and **next** vectors.

http://www.sunburst-design.com/papers/CummingsSNUG2003SJ_SystemVerilogFSM_rev1_1.pdf

Rincon Research Corporation - FPGA Development 20

LOGIC FOUNDRY Verilog one-hot encoding

```

module fsm_ccl_3oh (output reg rd, ds, input
go, ws, clk, rst_n);
parameter
IDLE = 0,          always @(posedge clk or negedge
READ = 1,          rst_n)
DLV = 2,          if (!rst_n) begin
DONE = 3;         rd <= 1'b0;
reg [3:0] state, next; ds <= 1'b0;
always @(state or go or ws) begin end
next = 4'b0;      else begin
case (1'b1)       state[IDLE] : if (go) next[READ] = 1'b1; rd <= 1'b0;
                  else next[IDLE] = 1'b1; ds <= 1'b0;
state[READ] :    next[DLV] = 1'b1; case (1'b1)
state[DLV] :    if (!ws) next[DONE] = 1'b1; next[READ] : rd <= 1'b1;
                  else next[READ] = 1'b1;
state[DONE] :    next[IDLE] = 1'b1;
endcase
endcase
end

```

Rincon Research Corporation - FPGA Development 21

LOGIC FOUNDRY FPGA Details

- 4-input LUT's
 - Attempt to architect logic into a pipeline of 4-bit inputs
- SRL/FIFO
 - Building shift registers or FIFO's from LUT's can be much cheaper than "simpler" solutions using registers
 - An 8-bit shift register can be done in one LUT, but requires 8 flip-flops + routing resources.
- Carry-chains
 - Ripple carry adders are typically much faster in an FPGA than an "faster" adder such as a carry lookahead as the carry chains are built into the fabric of the FPGA
- Block Rams
- Multipliers
- Power PC
- ???

Rincon Research Corporation - FPGA Development 22

LOGIC FOUNDRY Implementation Choices

- Duplicating Flip-Flops
- Coding styles for speed
- Selection instead of Evaluation
 - throw silicon at it
- Instantiate Target Technology primitives

Rincon Research Corporation - FPGA Development 23

LOGIC FOUNDRY Duplicating Flip-Flops

- High-fanout nets can be slow and hard to route
- Duplicating flip-flops can fix both problems
 - Reduced fanout shortens net delays
 - Each flip-flop can fanout to a different physical region of the chip to help with routing
- Design tradeoffs
 - Gain routability and performance
 - Design area increases

The diagram shows two scenarios. The top scenario shows a single flip-flop (labeled 'fn1') with its 'q' output connected to a long, multi-bit bus. The bottom scenario shows two flip-flops (both labeled 'fn1') with their 'q' outputs connected to two separate, shorter buses, each connected to a different physical region of the chip.

Rincon Research Corporation - FPGA Development 24


LOGIC FOUNDRY **Tips on Duplicating Flip-Flops (Xilinx)**

- Name duplicated flip-flops `_a, _b`: *NOT* `_1, _`
 - Numbered flip-flops are mapped by default into the same slice
 - You generally want duplicated flip-flops to be separated
 - Especially if the loads are spread across the chip
- Explicitly create duplicate flip-flops in your HDL code
 - Most synthesis tools have automatic fanout-control features
 - However, they do not always pick the best division of loads
 - Also, duplicated flip-flops will be named `_1, _2`
 - Many synthesis tools will optimize-out duplicated flip-flops
- Do not duplicate flip-flops that are sourced by asynchronous signals
 - Synchronize the signal first
 - Feed synchronized signal to multiple flip-flops

Rincon Research Corporation - FPGA Development 25

LOGIC FOUNDRY **Duplicating Flip-Flops Example**

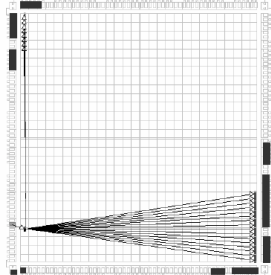
- Source flip-flop drives two register banks that are constrained to different regions of the chip
- Source flip-flop and pad are not constrained
- PERIOD = 5 ns timing constraint
- Implemented with default options
- Longest path = 6.806 ns
 - Fails to meet timing constraint



Rincon Research Corporation - FPGA Development 26

LOGIC FOUNDRY **Duplicating Flip-Flops Example**

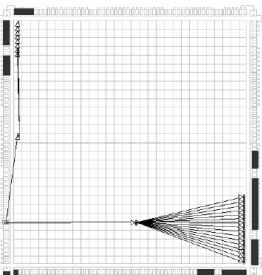- Source flip-flop has been duplicated
- Each flip-flop drives a region of the chip
 - Each flip-flop can be placed closer to the register that it is driving
 - Shorter routing delays
- Longest path = 4.666 ns
 - Meets timing constraint



Rincon Research Corporation - FPGA Development 27

LOGIC FOUNDRY **Duplicating Logic**

- Similar to the above example, but rather than simply duplicating flip-flops, sometimes it is necessary to duplicate entire sections of logic

Rincon Research Corporation - FPGA Development 28

LOGIC FOUNDRY **Coding Styles for speed**

- **Avoid Nested IF and CASE Statements**
 - Nested IF or CASE statements infer cascaded logic
 - More levels of logic = lower performance
- **Evaluate late-arriving signals last**
 - When nested IFs are necessary, put critical input signals on the first (outer) IF statement
 - The critical signal ends up in the last logic stage

Rincon Research Corporation - FPGA Development 29

LOGIC FOUNDRY **Select rather than Evaluate**

- Sometimes it is faster to select from all possible outcomes than it is to compute the correct outcome
 - Rather than wait for this 2-bit signal to arrive


```
acc <= acc + 2bit_signal ;
```
 - Compute all possibilities and use the control as an output selector


```
o1 <= acc + 00;
o2 <= acc + 01;
o3 <= acc + 10;
o4 <= acc + 11;
case (2bit_signal) begin
00: acc <= o1;
01: acc <= o2;
...
```

Rincon Research Corporation - FPGA Development 30

LOGIC FOUNDRY **Instantiate when speed needed**

- Xilinx says ...
 - Use instantiation only when it is necessary to access device feather or increase performance or decrease area
 - Limit the location of instantiated components to a few source files to make it easier to locate these components when porting the code
- So, we use instantiation frequently
 - It is almost always necessary to increase performance
 - Reusable code is a bit of a myth

Rincon Research Corporation - FPGA Development 31

LOGIC FOUNDRY **Synthesis Optimizations**

- **Pipelining**
 - Certain tools allow automatic pipelining of Xilinx multipliers and ROM's
- **Retiming**
 - We have discussed this
- **Overconstraining**
 - Always overconstrain the synthesis tool as they are never correct. Period.
 - Do not pass these constraints on to the layout tools – use the correct constraints in layout

Rincon Research Corporation - FPGA Development 32

LOGIC FOUNDRY Place and Route Optimizations

- Floorplanning
 - ENIAC example
- RPM's (relationally placed macros)
- Custom Placement
- Multi-Pass Place and Route

Rincon Research Corporation - FPGA Development 33

LOGIC FOUNDRY RPM's

Figure 2: 18 X 18 Multiplier Floorplan

Rincon Research Corporation - FPGA Development 34

LOGIC FOUNDRY Summary

- Algorithmic changes
 - By FAR, the most significant
- Architecture choices
- Implementation choices
- Synthesis Optimizations
- Place and Route Optimizations

Rincon Research Corporation - FPGA Development 35